 



## Memory Interconnection (Vertical Expansion)

Typical RAM chip.




CS1	$\overline{\text{CS2}}$	RD	WR	Memory function	State of data bus
0	0	x	x	Inhibit	High-impedance
0	1	x	x	Inhibit	High-impedance
1	0	0	0	Inhibit	High-impedance
1	0	0	1	Write	Input data to RAM
1	0	1	x	Read	Output data from RAM
1	1	x	x	Inhibit	High-impedance

Function table

 

Typical ROM chip.

 

Q. SUPPOSE WE HAVE 2 SETS OF MEMORIES WITH RAM OF SIZE  $128 \times 8$  AND ROM OF SIZE  $512 \times 8$ , we need to design a memory of capacity  $1024 \times 8$ . Draw the memory mapping table.

Solution:

FOR EACH RAM ( $128 \times 8$ ):

ADDRESS BUS SIZE = 7 BITS

DATA BUS SIZE = 8 BITS

FOR ROM ( $512 \times 8$ ):

ADDRESS BUS SIZE = 9 BITS

DATA BUS SIZE = 8 BITS

VERTICAL/ HORIZONTAL

SMALLEST ADDRESS (RAM) – 0

LARGEST ADDRESS (RAM) – 127

SMALLEST ADDRESS (ROM) – 0

LARGEST ADDRESS (ROM) – 511

For the required expanded memory size 1024 X 8 (EXPANDED)

SMALLEST ADDRESS (EXPANDED) = 0

LARGEST ADDRESS (EXPANDED) = 1023

ADDRESS BUS SIZE ((EXPANDED) = 10

DATA BUS SIZE (EXPANDED) = 8

Memory Mapping Table:

ITEMS	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
-------	----	----	----	----	----	----	----	----	----	----

RAM1	1/0	0	0	X	X	X	X	X	X	X
RAM2	1/0	0	1	X	X	X	X	X	X	X
RAM3	1/0	1	0	X	X	X	X	X	X	X
RAM4	1/0	1	1	X	X	X	X	X	X	X
ROM	0/1	X	X	X	X	X	X	X	X	X

Vertical Expansion:

Memory Interconnection Diagram for a 16 bit CPU

